

UNIT - 5

Thyristors and other Devices

The family of Thyristor are

1) PNP_N (Shockley Diode)

2) SCR (Silicon control Rectifier)

3) LASCR (Light Activated Silicon control Rectifier)

4) TRIAC (Triode as AC switch)


5) DIAC (Diode as AC switch)

6) UJT (unipolar Junction transistor)


7) IGBT (Insulated Gate Bi-Polar Transistor).

1) PNP_N (Shockley Diode) :-


fig(a) PNP_N - Basic structure

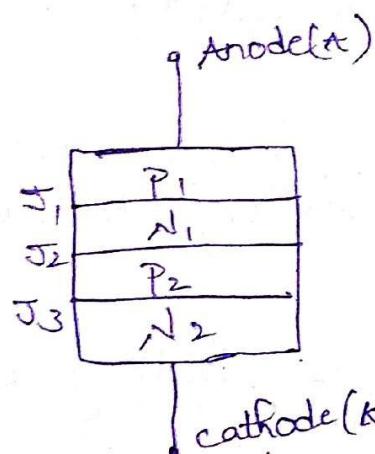

fig(b) Circuit symbol of PNP_N Diode :-

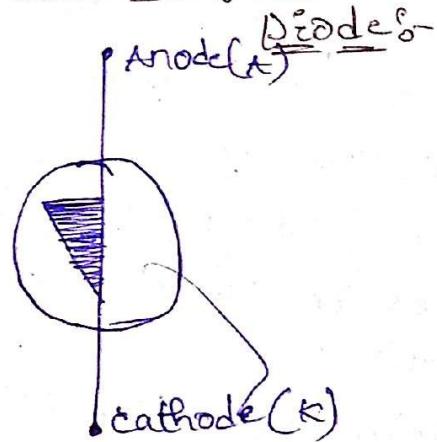

fig(c) Characteristics of PNP_N Diode :-

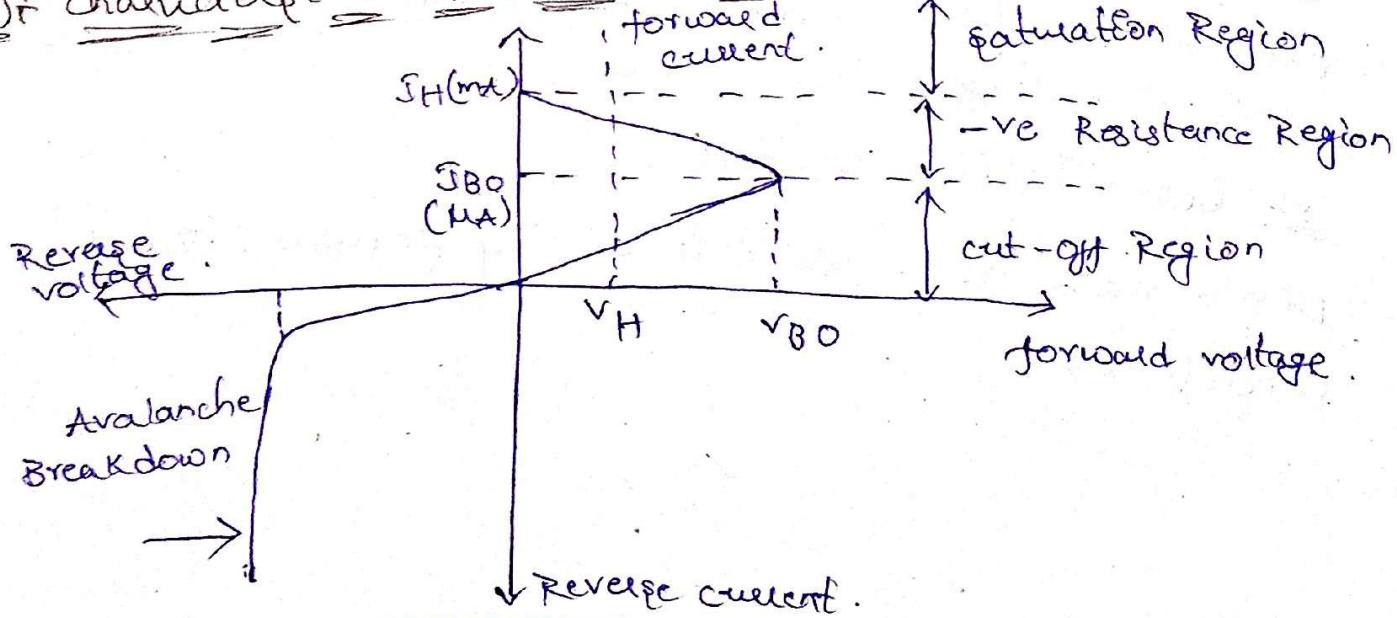

- Thyristor in general is a semiconductor device having three or more junctions
- Such a device acts as a switch without any bias & voltage ratings of several hundred volts & current ratings several hundred volts and current ratings of almost thousand amperes.
- family of thyristors consists of power diode (shockley diode), SCRs, LSCR, TRIAC, DIAC, UJT etc.
- As shown in fig, it is four layers p-type silicon device with two terminals.
- When an external voltage is applied to the device from anode to cathode junctions J_1 & J_3 are forward biased & J_2 is reverse biased.
- Current flowing is only reverse saturation current.
- As applied voltage is fed, current also rises slowly until so called firing or breakover voltage (V_{BO}) is reached.
- Once firing takes place current rises whereas voltage across which diode switches from "off" to "on" state.
- minimum amount of current known as holding current (I_H) is flown to keep in 'on' state.
- current has to be reduced below I_H by reducing applied voltage close to zero, not below holding voltage, V_H .
- Diode acts as a switch during forward bias condition.



Thyristor Ratings:

- 1) Latching current (I_L): the minimum current is required to latch (or) trigger the device from its off-state to on-state.
- 2) Holding current (I_H): minimum value of current to hold the device in on-state. for turning off, anode current should be lowered below I_H by increasing external circuit resistance.
- 3) Gate current (I_g): current applied to the gate of device for control purposes.
- 4) voltage safety factor (V_f): value of V_f normally lies b/w 2 and 2.7

$$V_f = \frac{PSV}{\sqrt{2} \times R_{rms} \text{ value of operating voltage}}$$

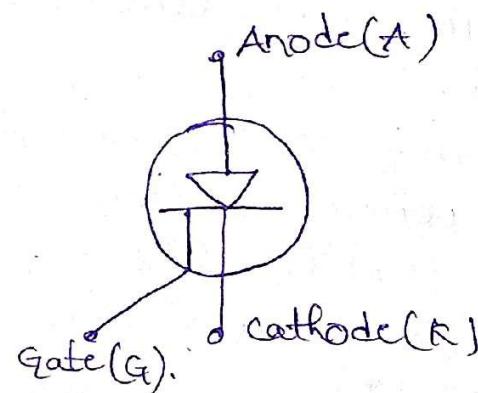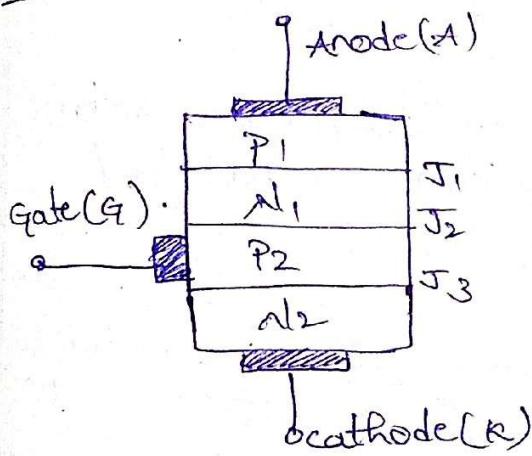2) SCR (Silicon Controlled Rectifier)


fig(a): Basic structure of SCR; fig(b): circuit symbol of SCR



It is a four layer, three terminal in which end p-layer acts as anode, end n-layer acts as cathode and p-layer nearer to cathode acts as gate.


As leakage current in Si is very small when compared to Ge, SCR's are made of Si & not Ge.

fig(c): characteristics of SCR

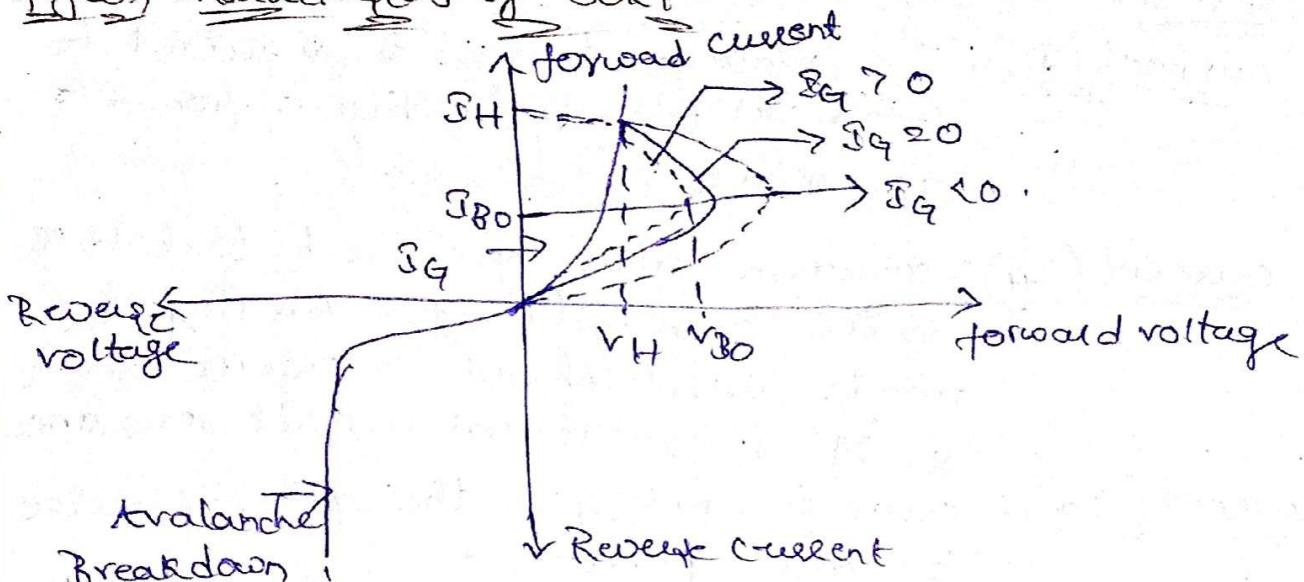


- * SCR acts as a switch when it is forward biased.
- * When gate is kept open with large jet gate current $I_G > 0$, operation of SCR is similar to normal diode.
- * When $I_G < 0$, amount of Reverse bias is applied to J_2 is fed there by V_{BO} breakdown voltage.
- * The voltage at which SCR is switched 'on' can be controlled by varying Gate current I_G , commonly known as controlled switch.
- * SCR is used in Relay control, motor control, phase control, heater control, battery charges, inverters, regulated power supplies & static switches.

fig(d): Two transistor version of SCR

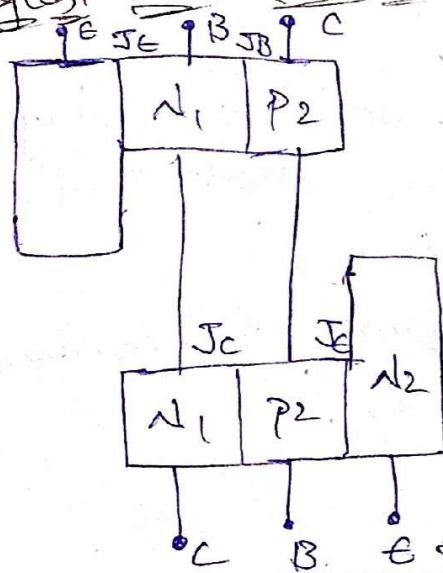

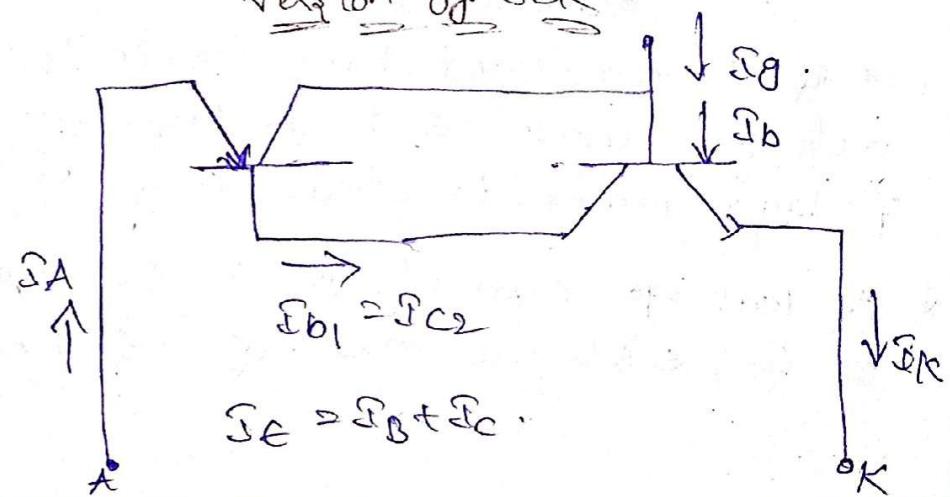fig(e): Equivalent circuit of two transistor version of SCR



* Operation of SCR is a simple way in terms of two transistors called as two transistor region of SCR.

* As shown in fig. (d), an SCR can be split into two parts and displaced from one another but connected electrically.

* Device may be considered by two transistors T_1 (PNP) & T_2 (NPN) connected back to back.

* Assuming leakage current of T_1 to be negligibly small, we get.

$$I_{b1} = I_A - \beta e_1 = I_A - \alpha I_A^2 (1 - \alpha_1) I_A \rightarrow (1)$$

$$\text{from eq's } I_{b1} = I_{C2} \rightarrow (2)$$

$$I_{C2} = \alpha_2 I_K \rightarrow (3)$$

By substituting eq's $\rightarrow (1)$ & (3) in eq (2) , we get

$$(1 - \alpha_1) I_A = \alpha_2 I_K \rightarrow (4)$$

$$w.k.t. I_K = I_A + I_B \rightarrow (5)$$

By substituting eq (5) in eq (4) we get

$$(1 - \alpha_1) I_A = \alpha_2 (I_A + I_B)$$

$$I_A = \left[\frac{\alpha_2 I_B}{1 - (\alpha_1 + \alpha_2)} \right] \rightarrow (6)$$

* This characteristics of device is known as regenerative action.

SCR Applications


1) SCR Half wave Rectifier

* Though SCR is basically a switch can be used in linear applications like rectification.


* During -ve half cycle, SCR does not conduct irrespective of gate current.

* As anode is -ve with respect to cathode & also V_A is less than reverse breakdown voltage.

fig(a) & circuit diagram of

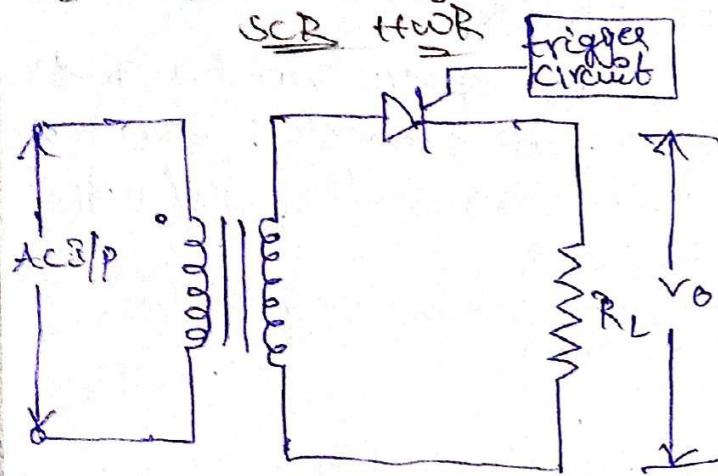

fig(b) of waveform of SCR FWR

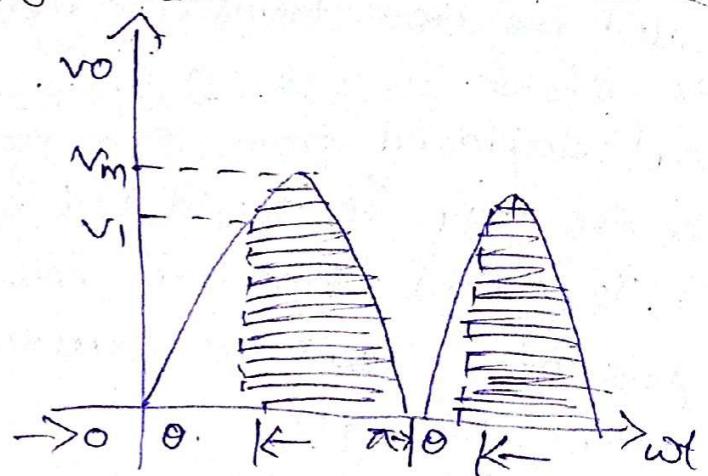

* During the half cycle, SCR conducts which provides proper gate current to flow.

* Greater the gate current, lesser the supply at which SCR is triggered on.

* SCR will be conducting till applied voltage becomes zero.

* Angle at which SCR starts conducting during the half cycle is called as firing angle θ .

* A conduction angle is $(180^\circ - \theta)$.

* If angle θ is zero, this will be an ordinary half wave rectification.

$$V_{avg} = \frac{1}{2\pi} \int_0^{\pi} V_m \sin \omega t d(\omega t)$$

$$= \frac{1}{2\pi} [-V_m \cos \omega t]_0^{\pi} = \frac{V_m}{2\pi} (1 + \cos \theta)$$

$$\text{for } \theta = 0^\circ \quad V_{avg} = \frac{V_m}{\pi}$$

$$\text{for } \theta = 90^\circ \quad V_{avg} = \frac{V_m}{2\pi}$$

2) SCR full wave Rectifier

* Exactly similar to that of ordinary FWR except that two diodes have been replaced by two SCR's.

* Angle of conduction can be changed by adjusting gate current.

* During the half cycle of E/P signal, anodes of SCR become +ve & at same time anode of SCR becomes -ve.

* SCR starts conducting & only shaded portion of the half cycle will pass through load.

- * During -ve half cycle of I/P signal, anode of SCR₁ becomes -ve & anode of SCR₂ becomes +ve.
- * Main advantage of this circuit over ordinary PWR is that any voltage can be made available at O/P by simply changing firing angle of SCR's

$$V_{avg} = \frac{1}{\pi} \int v_m \sin \omega t dt$$


$$= \frac{v_m}{\pi} [-\cos \omega t] \Rightarrow \frac{v_m}{\pi} (1 + \cos \omega)$$

$$V_{avg} = \frac{v_m}{\pi} (1 + \cos \omega)$$


- * It is double that of HWR, as -ve half cycle is also rectified.

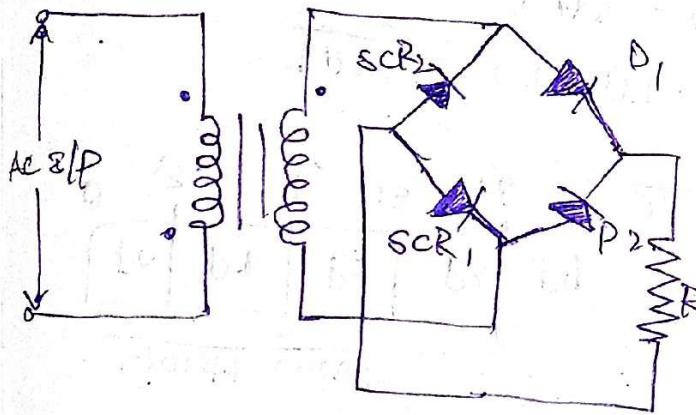3) SCR Bridge Rectifier

fig(a) Circuit diagram of SCR Bridge Rectifier



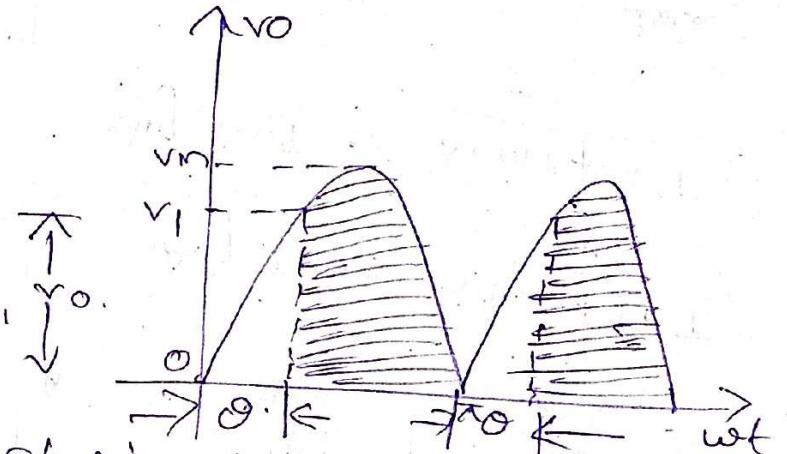fig(b) O/P waveform of SCR Bridge Rectifier



- * During +ve half cycle of I/P signal, SCR₁ & Diode D₁ conduct where SCR₂ & Diode D₂ does not conduct.
- * During -ve half cycle of I/P signal, SCR₂ & Diode D₂ conduct where SCR₁ & Diode D₁ does not conduct.


* Conduction angle and hence O/P voltage can be changed by adjusting gate currents of SCR₁ & SCR₂.

* D.C O/P voltage (a) $V_{avg} = \frac{v_m}{\pi} (1 + \cos \omega)$ which is equal to that of SCR-PWR

* If current is lowered below IT by increasing external circuit resistance, then SCR will switch off.

3) LASCR (Light Activated Silicon Controlled Rectifier)

Fig a) Light Activated SCR

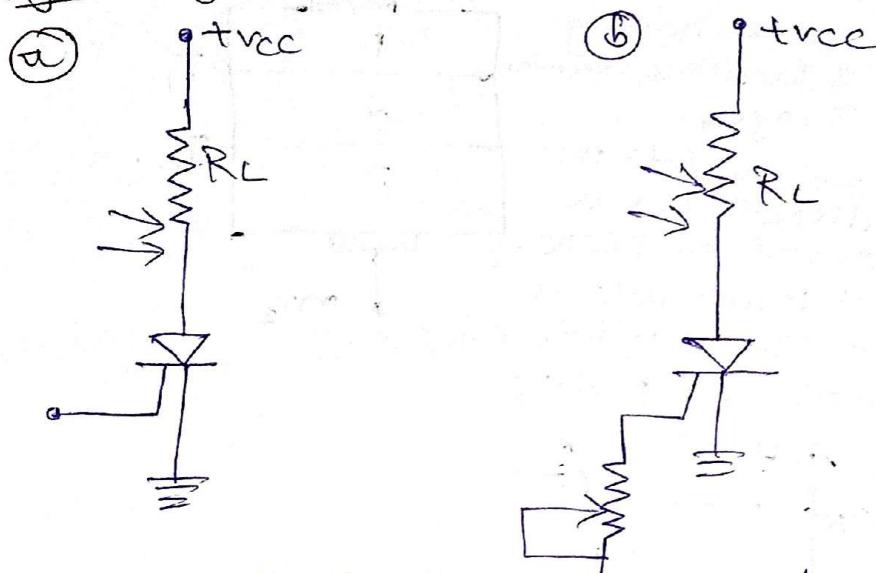


- * As shown in the figure LASCR is triggered by irradiating with light.
- * Arrow represents incoming light that passes through window & fall on depletion layer closer to middle junction J_2 of SCR.
- * Incident light generates electron hole ($e^- h$) pairs in the device thus increasing number of charge carriers.
- * This leads to instantaneous flow of current within the device & it turns on.
- * For light triggering to occur, device must have high value of rate of change of voltage with time, dv/dt .


4) TRIAC (Triode as a AC Switch) :-

- * Triac is a three terminal semiconductor switching device which can control alternating current in a load.
- * Its three terminals are MT₁, MT₂ & gate(s).
- * Basic structure & circuit symbol of triac are shown in fig a & fig b
- * TRIAC is equivalent two SCR's connected in parallel but in reverse direction as shown in figure.

(a) Basic structure


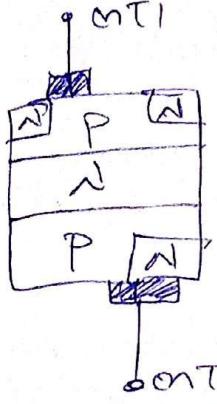


(b) Circuit symbol

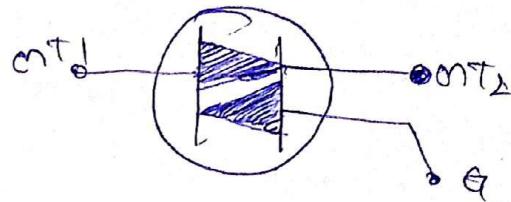


- * Both TRIAC well act as a switch for both directions.
- * Two SCR region TRIAC

Basic structure

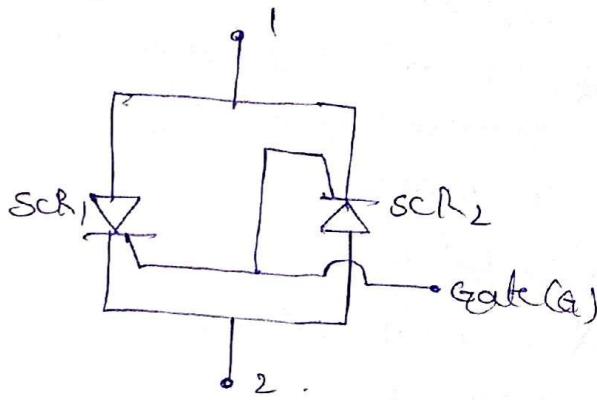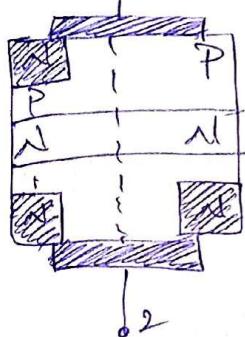

(c) Characteristics of TRIAC

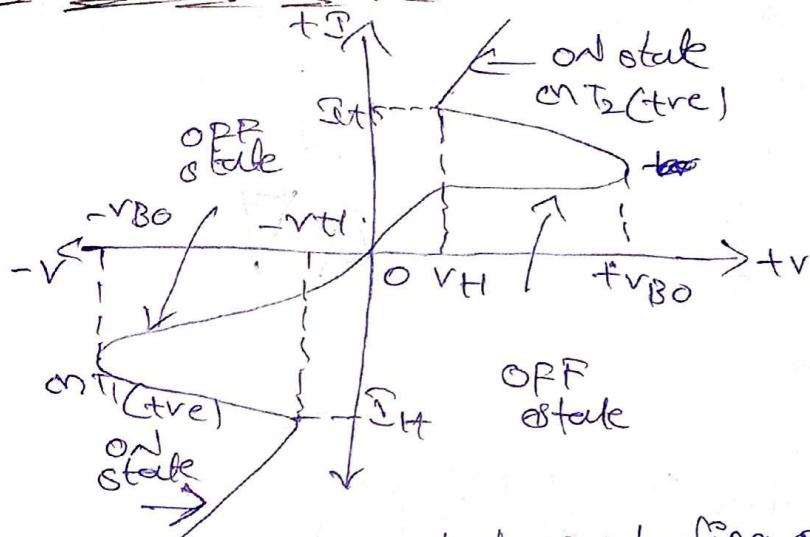

- * The SCR TRIAC also starts conducting only when break over voltage is reached.
- * Device when starts conducting allows very heavy amount of current to flow through it.
- * High current must be produced using external resistance otherwise device will be damaged.


- * During the half-cycle MT₁ is the comm. MT to which MT₂ is the comm. MT during the half cycle.
- * Triac is bi-directional device & can be triggered either by +ve or by -ve gate signal.
- * By applying proper signal at gate breakdown voltage can be changed thus phase control process can be achieved.
- * used for illumination control, temperature control, liquid level control, motor speed control & as static switch to turn power on & off.
- * Now-a-days, dia & triac pairs are fed to be replaced by a single component units known as quadrae.

Limitsations:


- * In comparison to SCR it has low power handling capacity.

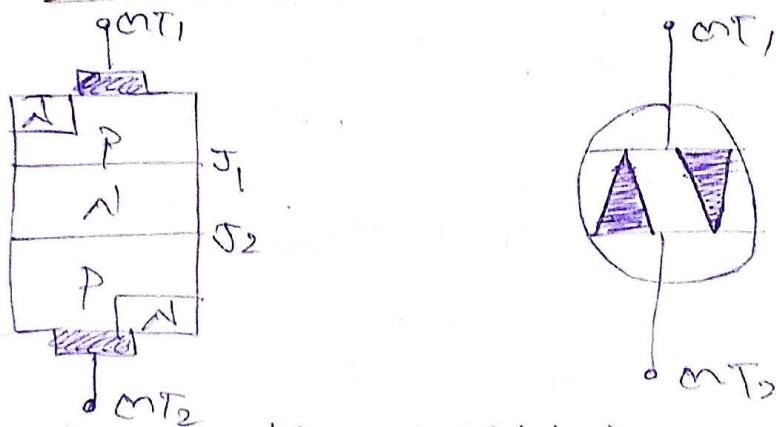5) DIAC (Diode as a AC switch)

Fig(a) DIAC Basic structure & Fig(b) Circuit symbol



Fig(c) Characteristics of DIAC:

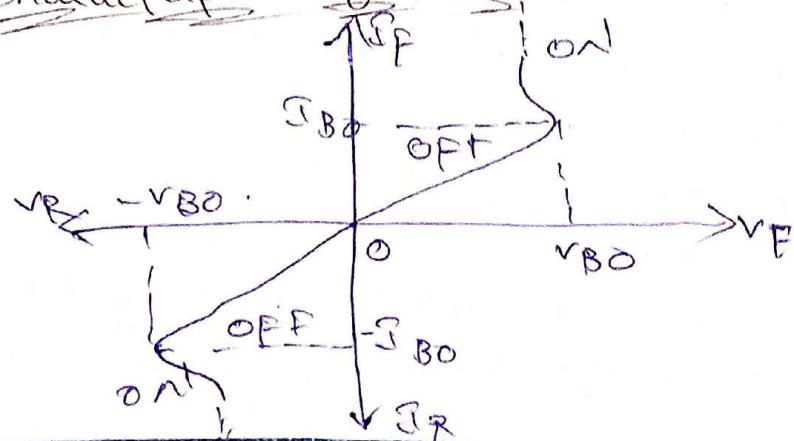


- * Construction & symbol of diac are shown in fig @ 25
- * It is a three layer, two terminal semiconductor device.
- * MT₁ & MT₂ are two main terminals which are interchangeable.
- * acts as bi-directional Avalanche diode
- * does not have any control terminal
- * does not have any control terminal
- * Has two functions J₁ & J₂
- * Diac resemble a bipolar transistor but central layer is free from any connection with terminal
- * From characteristics of Diac show in fig @ act as a switch in both directions
- * As doping level at two ends of device is same, diac has identical char's for both +ve & -ve half of A.C cycle.
- * During +ve half cycle, MT₁ is the wrt MT₂ where as MT₂ is the wrt MT₁ in -ve half cycle.
- * At voltage level reaches breakover voltage, device starts conducting & exhibits -ve resistance characteristics
i.e. current \propto s & voltage \downarrow s.
- * DIAC is not a control device.
- * used as triggering device in triac, phase control circuits used for light dimming, motor speed control & heater control.

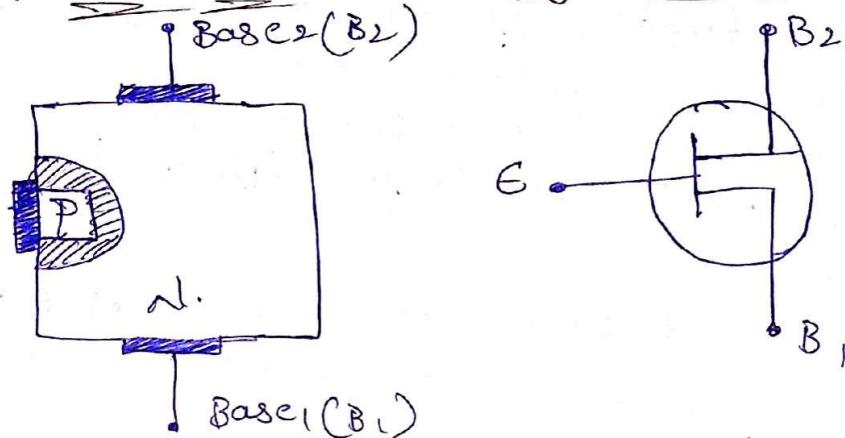6) UJT (uni-junction Transistor):


- * UJT is a three terminal semiconductor switching device
- * It has only one P-N junction & three leads, so it is commonly called as uni-junction transistor
- * It consists of a lightly doped N-type Si with a heavily doped P-type Si for producing single P-N junction
- * Circuit symbol of UJT is shown in fig (b).

fig(a): UJT Basic structure fig(b): Circuit symbol



* Arrow in fig -⑥ indicates direction of conventional.

fig(c): equivalent circuit:-

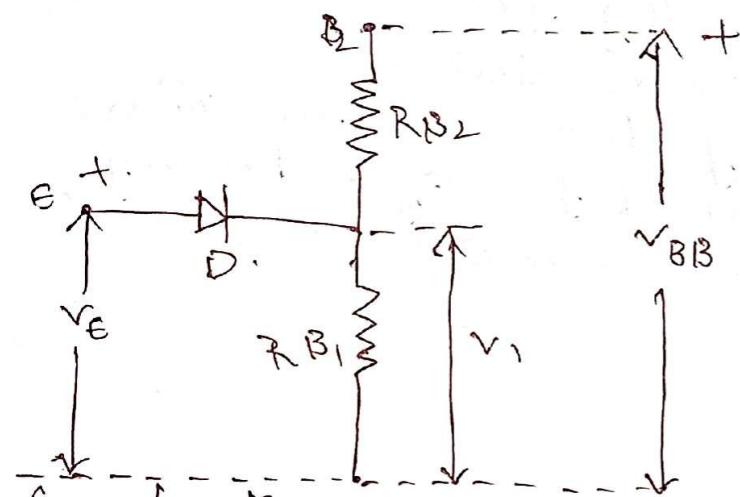

characteristics of UJT :-

* As shown in fig -⑦ Antebase resistance b/w B_2 & B_1 of Si is $R_{B1B} = R_{B1} + R_{B2}$

* with emitter terminal open, voltage v_{BB} is applied b/w two bases, a voltage gradient is established & voltage drop across R_{B1} is given by $v_i = n v_{BB}$

* where Intrinsic stand-off ration $n = \frac{R_{B1}}{R_{B1} + R_{B2}}$

* typical value of n ranges from 0.56 to 0.75

* voltage v_i reverse biases p-n Junction & it is cut-off

* If a +ve voltage v_E is applied to emitter p-n junction will remain Reverse Bias as long as $v_E < v_i$

* If v_E exceeds v_i ($v_E > v_i$) by cut-in voltage

* If v_E diode becomes forward bias

v_{D1} , Device now is in the 'on' state.

* If v_E Device now is in the 'on' state.

* If a -ve voltage is applied to the emitter, p-n junction remains Reverse Bias & it is cut-off

* Device now is in the 'off' state.

* upto the Peak Point P, the diode is R.B & hence to the left of peak point is called as cut-off Region.

* At P, peak voltage ($v_p = n v_{BB} + v_D$) diode starts conducting & holes are injected into n-layer.

* Hence, resistance \downarrow as there by \downarrow eng v_E for P-ing I_E .

* So, there is a -ve resistance region from peak point P to valley point V.


* Region to the Right of valley point is called saturation region.

* So, there is a +ve resistance

- * In the valley point, resistance changes from +ve to -ve
- * Resistance remains +ve in the saturation region

* for very large I_E , characteristic asymptotically approaches curve for $I_{B_2} = 0$.

Fig(d): I/P characteristics of VJT

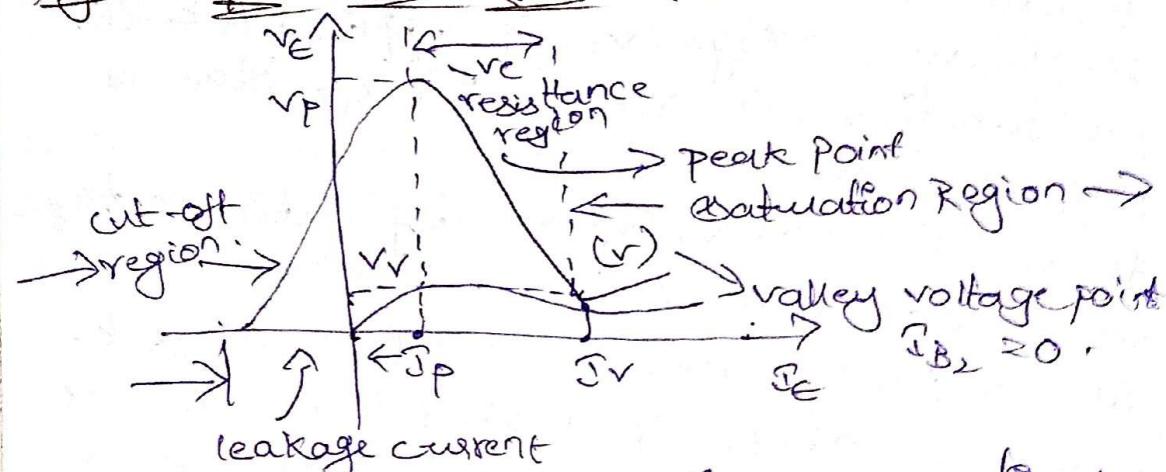


* When it is triggered, I_E increases regeneratively until it is limited by emitter power supply.


* Due to -ve resistance property, a VJT can be used for variety of applications such as sawtooth generator, pulse generator, switching, timing & phase control circuits.

VJT Relaxation oscillator




Fig(a) Circuit diagram:

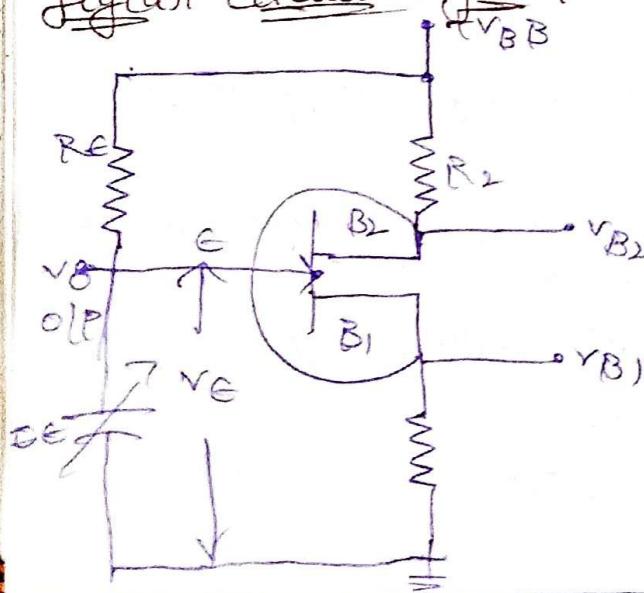

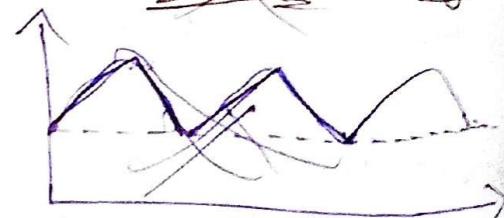Fig(b) VJT Relaxation oscillator waveform



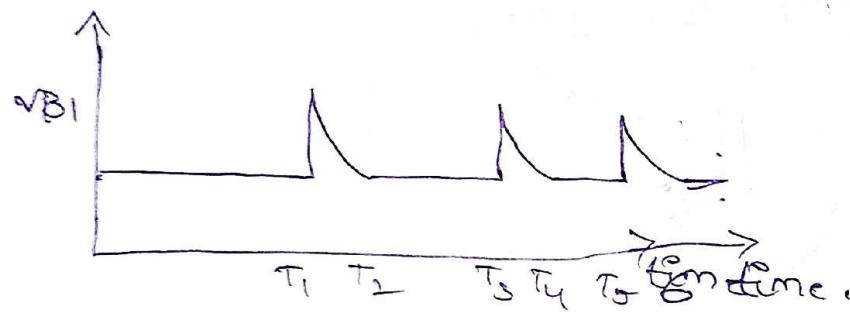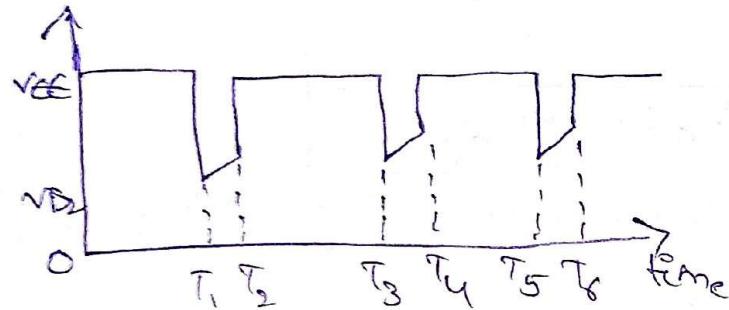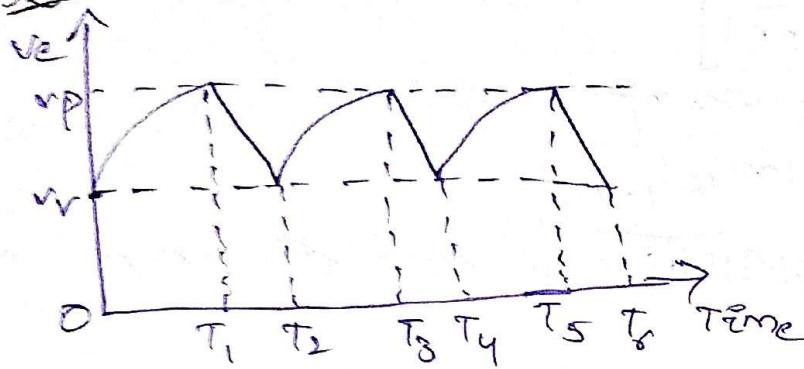fig(0) + UJT Relaxation oscillator waveform



* Relaxation oscillator using UJT for generating sawtooth waveform is shown in fig @.

* It consists of a UJT & a capacitor C_C charged through R_C as supply voltage V_{DD} is switched on.

* V_C across capacitor is given by
$$V_C = V_{DD} \left(1 - e^{-t/R_C C_C}\right)$$
 where $R_C C_C$ = charging time constant of resistor-capacitor ckt

t = time of the waveform.

* Discharge of capacitor occurs where $V_C = \text{peak-pf voltage}$ $\Rightarrow V_C = V_P = n V_{BB}$

$$\text{Let } V_C = n V_{BB} = V_{DD} \left(1 - e^{-t/R_C C_C}\right)$$

$$n = 1 - e^{-t/R_C C_C} \Rightarrow e^{-t/R_C C_C} = (1 - n)$$

General Time Period of OJT.

$$\therefore t = R_{CE} \log \frac{1}{(1-n)}$$

Time period when waveform occurs

$$\therefore t \geq 2 \cdot 303 R_{CE} \log \frac{1}{(1-n)}$$

frequency of oscillation of sawtooth wave
is given by

$$f = \frac{1}{T} = \frac{1}{2 \cdot 303 R_{CE} \log \frac{1}{(1-n)}}$$

7) IGBT (Insulated-Gate Bipolar Transistor)

(a) Circuit Symbol for IGBT:


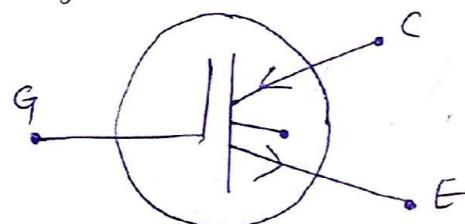


Fig b:- Equivalent ckt for IGBT:

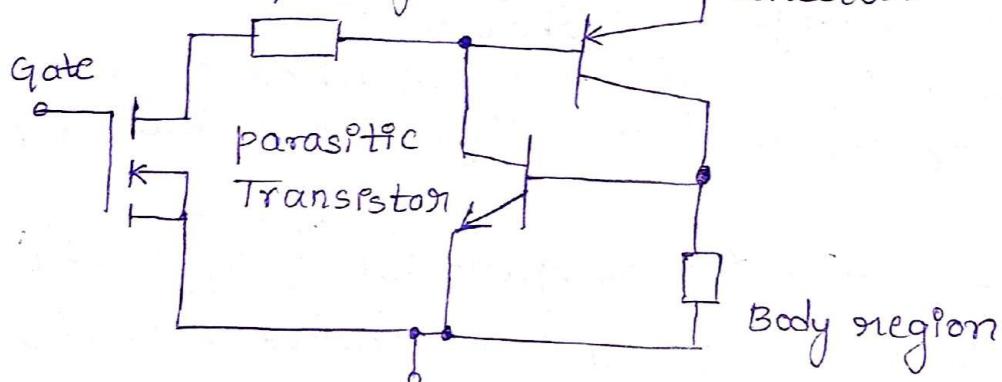

* IGBT is a three terminal power semiconductor device mainly used as electronic switch.

* This switch is mainly developed to combine high efficiency and fast switching.

* It switches electric power in many modern appliances such as variable frequency drives (VFD's).

electric cars, trains, variable speed refrigerators, lamp ballasts, air-conditioners & even stereo systems.

* In switching applications ultrasonic range frequencies are at least 10^3 times the highest audio frequency when used as an analog audio amplifier.

* IGBT combines simple gate drive characteristics of MOSFET's with high current and low-saturation voltage of bipolar transistors. I_C

* IGBT combines an isolated gate FET for control input and bipolar power transistor as a switch in single device.

* IGBT is used in medium-to-high power applications such as switched mode power supplies, traction motor control & induction heating.

* Large IGBT modules typically consists of many devices in parallel and can have very high current in hundreds of amperes blocking voltages of 6000V and power is of kilowatts.

* IGBT's are important for electric vehicles and hybrid cars.

